

$$I = \frac{\Delta Q}{\Delta t} \quad \text{Ampere}$$

$$j = n v_d q$$


\rightarrow vel. deriva
 \rightarrow carica portatore
 \rightarrow dens. port.

$$v_d \ll v_{th}$$

$$I = j \cdot S$$

$$\vec{j} = n v_d \vec{q}$$

$$I = \int \vec{j} \cdot \vec{S}$$

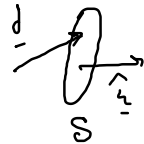

Materiali ohmici:

$$j = \sigma \vec{E}$$

\rightarrow Conduttività

// non ohmici:


j non è $\propto E$ (semiconduttori)

Legge di Ohm

$$j = \frac{I}{S}$$

$$\Delta V = \int E \cdot d_{AB}$$

\uparrow E uniforme

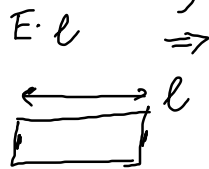

$$E = \frac{\Delta V}{l}$$

$$\underbrace{\frac{I}{S}}_j = \sigma \underbrace{\frac{\Delta V}{l}}_E$$

$$\Delta V = \frac{l}{S \sigma} \cdot I$$

$\frac{l}{S \sigma} \rightarrow R$: resistenza

$$\Delta V = RI$$

$$R = \frac{l}{S \sigma}$$

$$\frac{1}{\sigma} = \rho$$

$$[\Delta V] = V \quad [I] = A$$

R dipende



materiali σ
geometria

ρ : resistività

$$[R] = \frac{V}{A} = \Omega \quad \text{Ohm}$$

$$[\rho] = \left[\frac{R \cdot S}{l} \right] = \frac{\Omega \cdot m^2}{m} = \Omega \cdot m$$


materiale
ohmico

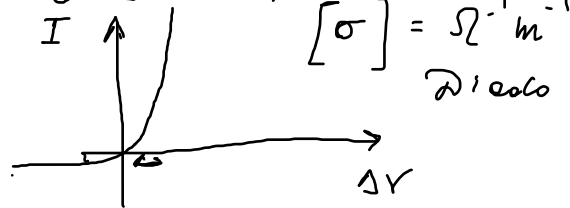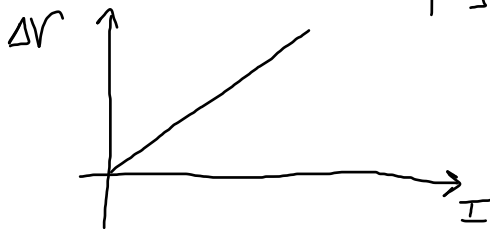

$$[\sigma] = \Omega^{-1} m^{-1}$$

dieci

Potenza elettrica

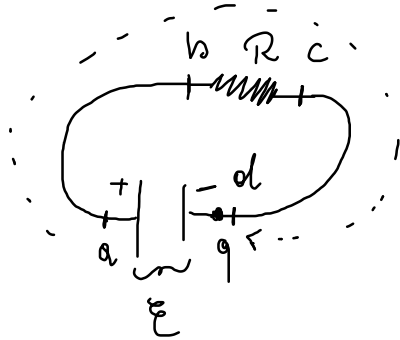

$$\Delta U_{\text{batt}} = q \mathcal{E}$$


$$\Delta U_{ab} = 0 \quad (a-b)$$

$$\Delta V_R = RI \quad \Delta U_R < 0 \quad (b-c)$$

$$\Delta U_{cd} = 0 \quad (c-d)$$

$$\Delta U_{\text{batt}} = q \mathcal{E} = \Delta U_R = q RI$$
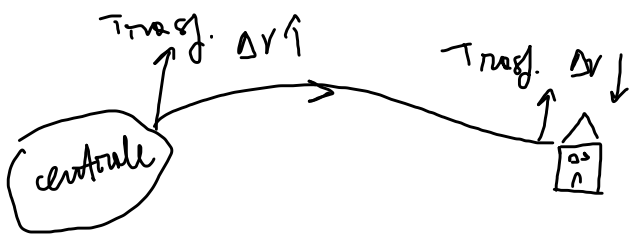
$$\begin{aligned} P &= \frac{d(\Delta U)}{dt} = \frac{d(qRI)}{dt} \quad \Delta V \cdot I \\ &= RI \frac{dq}{dt} = RI^2 = \frac{\Delta V^2}{R} \end{aligned}$$



$$P_{centrale} = P_{linea} + P_{utilizzatore}$$

$$P_{centrale} = \Delta V \cdot I$$


$$P_{linea} = R \cdot I^2$$

Alte tensioni
Basse correnti

Trasformatore

Cons. energia

Carica di un condensatore

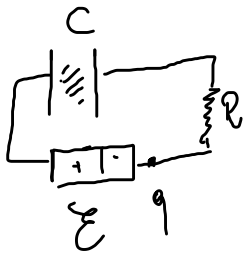

$$\Delta U_{batt} = q \cdot \mathcal{E}$$

$$\Delta U_{batt} = \Delta U_C + \Delta U_R$$

$$q \cdot \mathcal{E} = q \cdot \Delta V_C + q \cdot \Delta V_R$$

$$\mathcal{E} = \Delta V_R + \Delta V_C \quad \Delta V_R = R \cdot I$$

$$C = \frac{Q}{\Delta V_C}; \quad \Delta V_C = \frac{Q}{C}$$

variabili

$$\mathcal{E} = \underbrace{R \cdot I}_{\text{costanti}} + \underbrace{\frac{Q}{C}}_{\text{variabili}}$$

$$I(t)$$
$$Q(t)$$

$$I = \frac{dQ}{dt}$$

$$\mathcal{E} = R \frac{dQ}{dt} + \frac{Q}{C}$$

eq. di 1° ordine
a coeff. costanti

$$\mathcal{E}C = RC \frac{dQ}{dt} + Q;$$

$$\mathcal{E}C - Q = RC \frac{dQ}{dt};$$

$$\frac{dQ}{\mathcal{E}C - Q} = \frac{dt}{RC};$$

$$\frac{dQ}{Q - \mathcal{E}C} = \frac{-dt}{RC}$$

$$\frac{dQ}{dt} = -\frac{Q - \varepsilon C}{RC}$$

$Q - \varepsilon C$
dimensionale

$$[RC] = [RC] = s \quad \text{Tempo caratteristico}$$

$$\int_0^{Q(t)} \frac{dQ}{Q - \varepsilon C} = - \int_0^t \frac{dt}{RC}$$

$$\ln [Q - \varepsilon C] \Big|_0^{Q(t)} = - \frac{t}{RC}$$

$-t/RC$

$$\ln \left[\frac{Q(t) - \varepsilon C}{-\varepsilon C} \right] = - \frac{t}{RC}$$

$$\frac{Q(t) - \varepsilon C}{-\varepsilon C} = e^{-t/RC}$$

$$Q(t) = \varepsilon C \left[1 - e^{-t/RC} \right]$$

$$I(t) = \frac{dQ}{dt} = \frac{d}{dt} \left[\varepsilon C (1 - e^{-t/\tau}) \right]$$

$$= \frac{\varepsilon C}{\tau} e^{-t/\tau} = \frac{\varepsilon}{R} e^{-t/\tau} \quad Q(t) = \varepsilon C (1 - e^{-t/\tau})$$



$\tau \rightarrow RC$

$$\lim_{t \rightarrow +\infty} Q(t) = \varepsilon C$$

$$C = \frac{Q_{\max}}{\varepsilon} \rightarrow Q_{\max} = C \cdot \varepsilon$$

Q vale t^* si ha
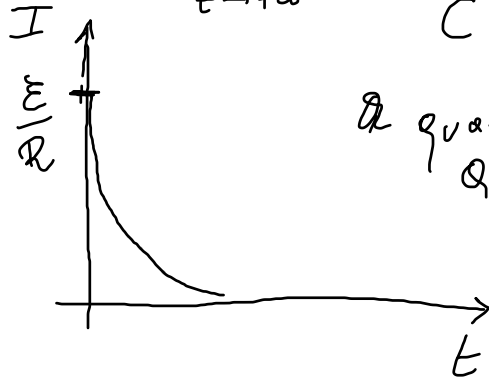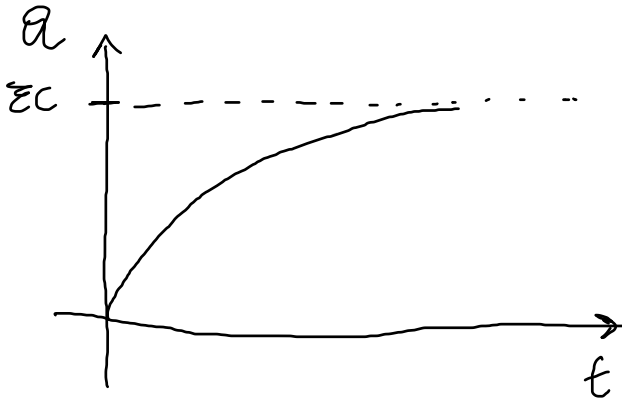
$$Q(t^*) = Q_{\max} = \frac{\varepsilon C}{2}$$



$$\frac{\cancel{\varepsilon} \varepsilon}{2} = \cancel{\varepsilon} \varepsilon (1 - e^{-t^*/\tau})$$

$$\underbrace{\vphantom{\frac{\varepsilon \varepsilon}{2}}}_{Q(t^*)} \quad \frac{1}{2} = e^{-t^*/\tau}$$

$$\tau = RC$$

$$-\ln 2 = \ln\left(\frac{1}{2}\right) = \ln\left(e^{-t^*/\tau}\right) = -t^*/\tau$$

$$t^* = \ln 2 \cdot \tau \approx 0.69 \cdot \tau$$

$$\tilde{t} \rightarrow 99\% Q_{\max}$$

$$\tilde{t} \approx 4.6 \tau$$

Se aspetto $t = 5\tau$

$$\rightarrow Q > 99\% Q_{\max}$$