




Resistance in series

$$R_{eq} = R_1 + \dots + R_m$$

Resistance in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \dots + \frac{1}{R_m}$$


ES m° 7 pag 858

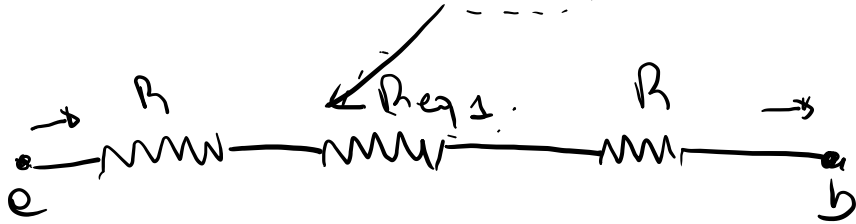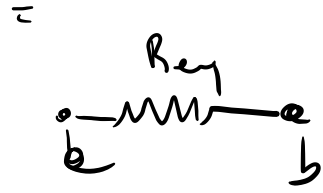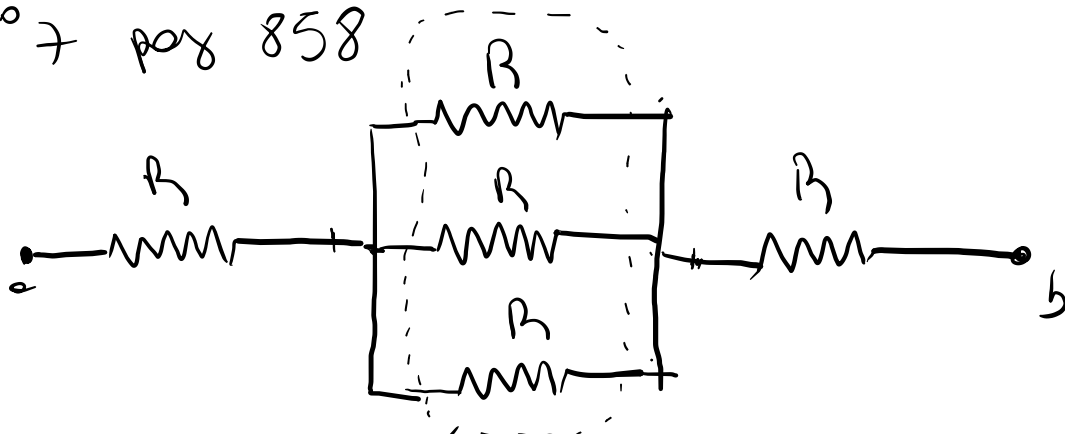

$$\frac{1}{R_{eq1}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{1}{R} = \frac{3}{R} \Rightarrow R_{eq1} = \frac{R}{3}$$

$$R_{eq_{TOT}} = R + \frac{R}{3} + R = \frac{7}{3} R$$

ES m°13 pag 859


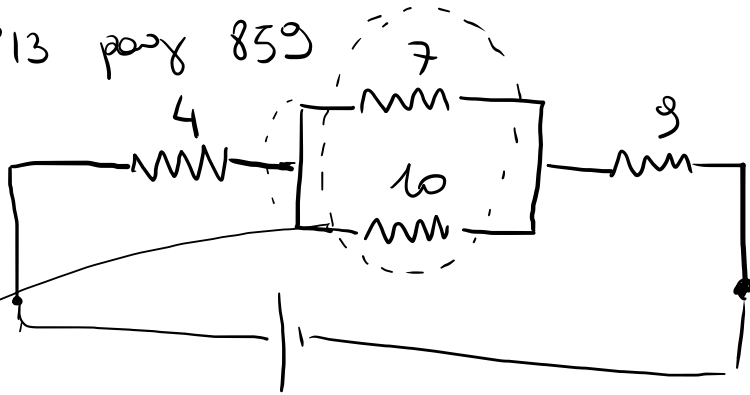


$R_{eq_{TOT}}$

de $\Delta V = 34V$

I cu cunoscuta rezistență

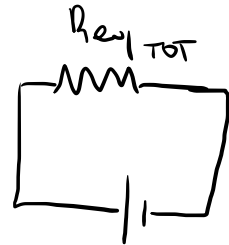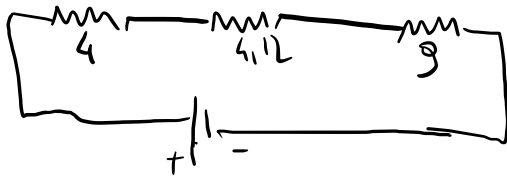
$$\frac{1}{R_{eq_1}} = \frac{1}{7} + \frac{1}{10} \Rightarrow R_{eq_1} = \frac{70}{17} = 4,12 \Omega$$



$$R_{eq_{TOT}} = 4 + 4,12 + 9 = 17,12 \Omega$$

$$\Delta V = I \cdot R$$
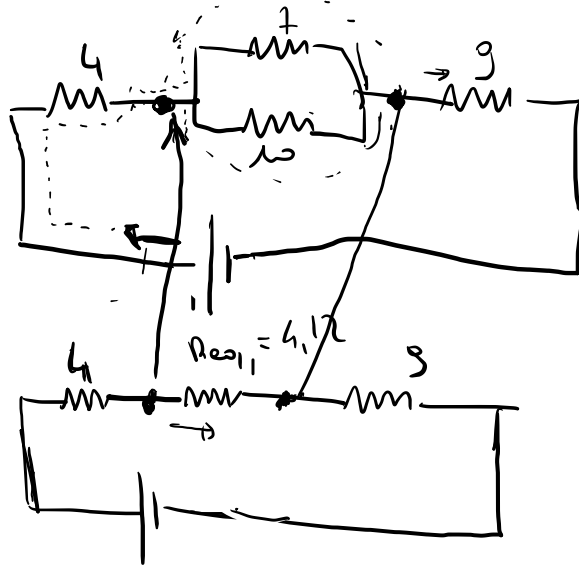
$$I = \frac{\Delta V}{R} = \frac{34}{17,1} \sim 1,99 \text{ A}$$



dalle resistenze da
4 e 9 Ω passa
tutte $I = 1,99 \text{ A}$

$$\Delta V = I \cdot R_{eq1} = 1,99 \cdot 4,12 = 8,18 \text{ V}$$

Dalle resistenze da 7 Ω
10 Ω


$$8,18 = I \cdot 7 \quad I = \frac{8,18}{7} = 1,17 \text{ A}$$

$$8,18 = I \cdot 10 \rightarrow$$


$$(1,99 - 1,17 = 0,818 \text{ A})$$

$$I_{\text{TOT}} = I_1 + I_2$$

ES m^o 18 pag 858

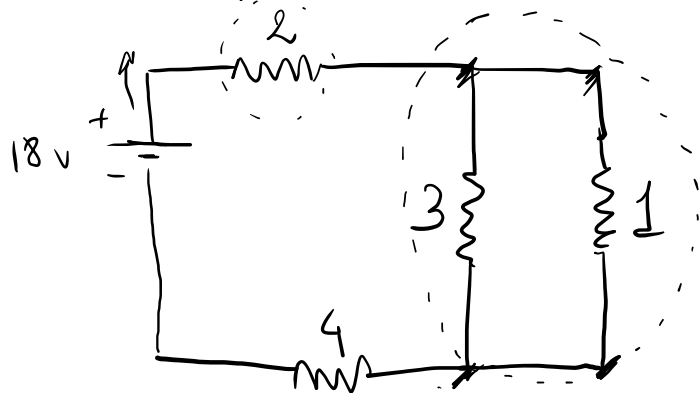

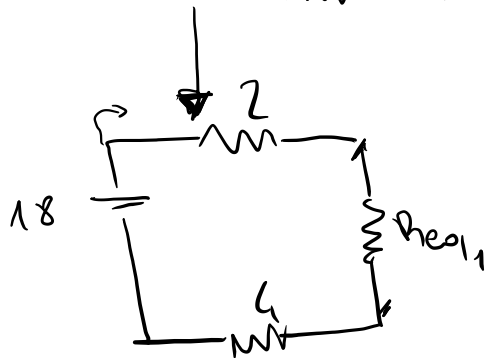Potenza dissipata
sulle uniche resistenze?




$$\Rightarrow \frac{1}{R_{eq1}} = \frac{1}{1} + \frac{1}{3} \rightarrow R_{eq1} = \frac{3}{4} = 0,75\Omega$$

$$R_{eq_{tot}} = 2 + 4 + 0,75 = 6,75\Omega$$

$$I = \frac{18}{6,75} = 2,67 \text{ A}$$

$$P_{20\Omega} = I^2 R = (2,67)^2 \cdot 2 = 14,2 \text{ W}$$
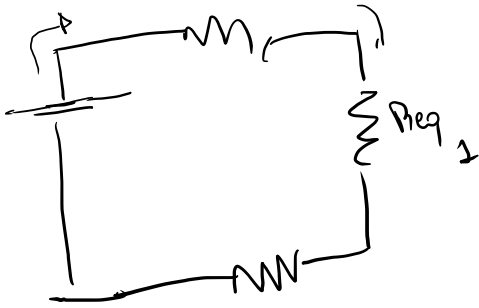
$$P_{40\Omega} = I^2 \cdot R = (2,67)^2 \cdot 4 = 28,4 \text{ W}$$



$$\begin{aligned} \Delta V &= I \cdot R_{eq1} \\ &= 2,67 \cdot 0,75 = 2 \text{ V} \end{aligned}$$

$$I_3 = \frac{\Delta V}{R_1} = \frac{2}{3} = 0,667 \text{ A}$$

$$P_3 = (0,667)^2 \cdot 3 = 1,33 \text{ W}$$

$$I_1 = \frac{2}{1} = 2 \text{ A}$$

$$I_{TOT} = 2,67 \text{ A}$$

$$\begin{aligned} I_2 &= I_{TOT} - I_1 \\ &= 2,67 - 0,67 = 2 \text{ A} \end{aligned}$$

$$P_{20\Omega} = 4 \cdot 1 = 4 \text{ W}$$

• Corrente e tensione di un condensatore
in un circuito RC



$$\tau = RC$$

$$Q = \varepsilon \cdot C$$

• CARICA

$$q(t) = Q \cdot (1 - e^{-t/\tau})$$

$$i = \frac{dq}{dt}$$

$$i(t) = \frac{\varepsilon}{R} e^{-t/\tau}$$

• tensione


$$v(t) = Q_i e^{-t/\tau}$$

$$i(t) = - \left[\frac{Q_i}{\tau} \right] e^{-t/\tau}$$

[corrente]

$\frac{Q_i}{\tau} = I_i$
corrente iniziale
nel circuito.

ES m° 38 pag 862

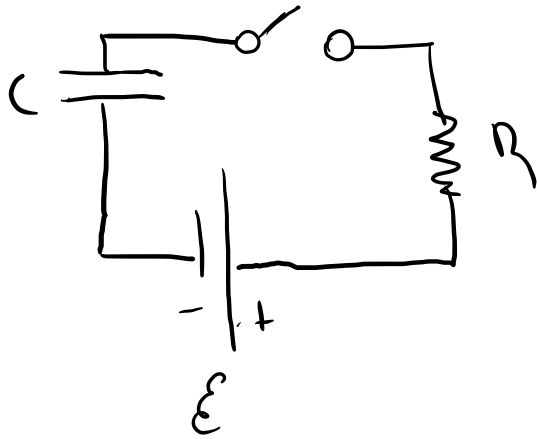

$$R = 1 \text{ M}\Omega$$

$$C = 5 \text{ }\mu\text{F}$$

$$\mathcal{E} = 30 \text{ V}$$


- 1- $\tau = ?$
- 2- $Q = ?$ carica massima su C
- 3- $i(t)$ dopo $t = 10 \text{ s}$

$$\tau = RC = 1 \cdot 10^6 \cdot 5 \cdot 10^{-6} = 5 \text{ s}$$

$$Q = C \Delta V = C \mathcal{E} = 5 \cdot 10^{-6} \cdot 30 = 150 \cdot 10^{-6} \text{ C}$$

$$\begin{aligned} i(t) &= \frac{\mathcal{E}}{R} e^{-t/\tau} = \left(\frac{30}{10^6} \right) \exp(-10/5) \\ &= 30 \cdot 10^{-6} \cdot 0,135 = 4,06 \cdot 10^{-6} \text{ A} \end{aligned}$$

ES n° 45 pag 862

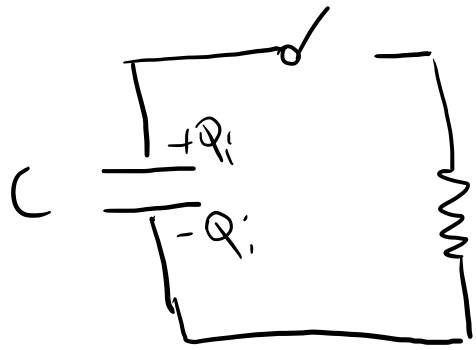

$$\tau = 1,5 \text{ s}$$

• dopo quanto tempo t dalle
cariche dell'initial
volta su C è 75%

• a $R = 250 \text{ k}\Omega$ quanto vale C

$$q(t) = Q_i e^{-t/\tau}$$

$$q(t) = 0,75 Q_i$$

$$e^{-t/\tau} = 0,75$$

$$\rightarrow 0,75 Q_i = Q_i e^{-t/\tau}$$

$$-t/\tau = \ln(0,75)$$

$$t = -\tau \ln(0,75)$$

$$= -1,5 \ln(0,75) = 0,432 \text{ s}$$

$$C \approx R = 250 \mu\Omega$$

$$\tau = 1,5 \text{ s}$$

$$\tau = RC$$

$$C = \frac{\tau}{R} = \frac{1,5}{250 \cdot 10^3} = 6 \cdot 10^{-6} \text{ F} = 6 \mu\text{F}$$

