

$$I_{\text{medie}} = \frac{\Delta Q}{\Delta t}$$



$$I = \frac{dq}{dt}$$

$$I = n \cdot q \cdot v_d \cdot A \quad J = I/A = n \cdot q \cdot v_d$$

conductivitate

$$J = \sigma E \quad \text{legea lui Ohm} \rightarrow \Delta V = R \cdot I$$

rezistentie

$$R = \frac{\Delta V}{I} \quad [\Omega]$$

resistivité  $\rightarrow$  qu'on soustraie le volume  $\rightarrow$   $\rho = \frac{1}{\sigma}$   
 pour la section

$$R = \rho \cdot \frac{l}{A}$$

$$P = \frac{dU}{dt} = \frac{d(Q \cdot \Delta V)}{dt} = \frac{dQ}{dt} \cdot \Delta V = I \cdot \Delta V$$

$\left. \begin{array}{l} \text{---} \\ \text{---} \\ \text{---} \end{array} \right\} \Delta V = R \cdot I$

$\downarrow$   
 $\sigma I^2 \cdot R$   
 $\sigma \frac{(\Delta V)^2}{R}$

ES mº 6 pag 826

$$r = 1,25 \text{ mm} \rightarrow \text{dado de nome}$$

$$I = 3,7 \text{ A}$$

$$v_d = ?$$

$$\leftarrow n = 8,46 \cdot 10^{28} \text{ e}^-/\text{m}^3$$

$$I = n \cdot q \cdot v_d \cdot A \rightarrow \pi r^2$$

$$v_d = \frac{I}{n q \pi r^2} = \frac{3,7}{(8,46 \cdot 10^{28}) \cdot (1,6 \cdot 10^{-19}) \pi \cdot (1,25 \cdot 10^{-3})^2}$$

o que quero é  $v_d$   
re m corrente

$$= \frac{3,7}{(8,46 \cdot 1,6 \cdot \pi \cdot 1,25) \cdot 10^3}$$

$$= \frac{3,7}{66,41} \cdot 10^{-3} = 0,0556 \cdot 10^{-3} = 5,56 \cdot 10^{-4} \text{ m/s}$$

ES m° 15 pag 826

$$l = 50 \text{ m}$$

$$d = 2 \text{ mm}$$

$$\Delta V = 9,11 \text{ V}$$

$$I = 36 \text{ A}$$

? di quale materiale è fatto il  
filo  $\rightarrow$  ossido che si è formato

$$\rightarrow R = \frac{\Delta V}{I} = \frac{9,11}{36} = 0,253 \Omega$$

$$R = \rho \cdot \frac{l}{A}$$

$$A = \pi r^2 = \pi \cdot (1 \cdot 10^{-3})^2 = \pi \cdot 10^{-6}$$

$$\rho = \frac{R \cdot A}{l} = \frac{0,253 \cdot \pi \cdot 10^{-6}}{50} = 1,59 \cdot 10^{-8} [\Omega \cdot \text{m}]$$

TABELLA 27.2 pag 814  $\rightarrow$  [ossigeno]

ES m<sup>o</sup> 18 pag 827

due fili  $\nearrow$  Cu  
 $\searrow$  Al

$$l_{Al} = l_{Cu}$$

$$R_{Al} = R_{Cu}$$

?  $v_{Al}/v_{Cu}$

$$R = \rho \cdot \frac{L}{A}$$

$$\rho_{Cu} \cdot \frac{L_{Cu}}{\pi r_{Cu}^2} = \rho_{Al} \cdot \frac{L_{Al}}{\pi r_{Al}^2} = \frac{v_{Al}^2}{v_{Cu}^2} = \frac{\rho_{Al}}{\rho_{Cu}}$$

$$\frac{v_{Al}}{v_{Cu}} = \sqrt{\frac{\rho_{Al}}{\rho_{Cu}}} = \sqrt{\frac{2.82 \cdot 10^8}{1.7 \cdot 10^8}} = 1.29$$

ES n° 39 pag 828

toute poutre cou une puissance = 1 kW

$$\Delta V = 120 \text{ V}$$

$$I = ?$$



$$R = ?$$

$$P = I \cdot \Delta V$$

$$I = \frac{P}{\Delta V} = \frac{1 \cdot 10^3}{120} = \frac{1000}{120} = 8,33 \text{ A}$$

$$R = \frac{\Delta V}{I} = \frac{120}{8,33} = 14,4 \Omega$$

• RESISTORI IN SERIE e in PARALLELO

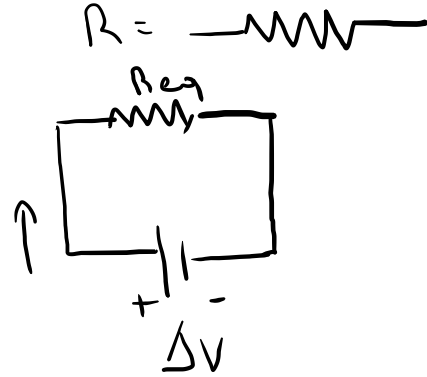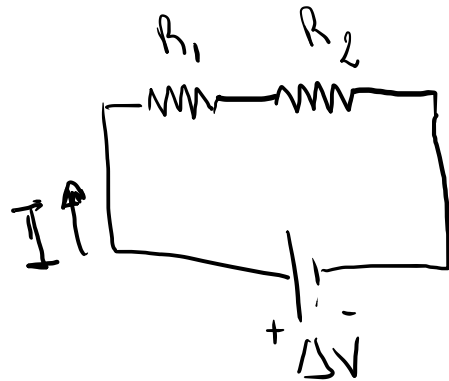

$I_1$   
 $I_2$  > è lo stesso ed uguale a  $I$

$$\Delta V = \Delta V_1 + \Delta V_2$$

$$= I_1 R_1 + I_2 R_2$$


$$= I R_1 + I R_2$$

$$\Delta V = R_{eq} \cdot I$$


$$R_{eq} \cdot I = I \cdot R_1 + I R_2$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$
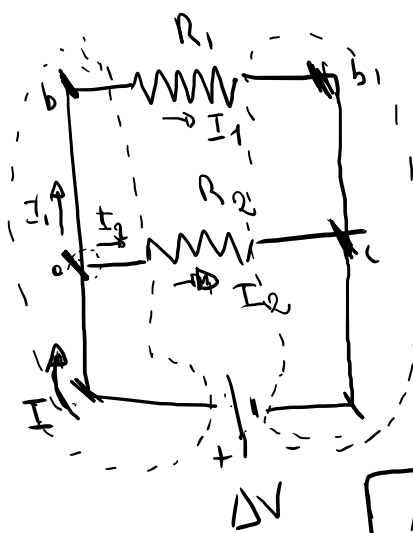
$$\Delta V_{bc} = \Delta V_{bd} \\ = \Delta V$$



=>

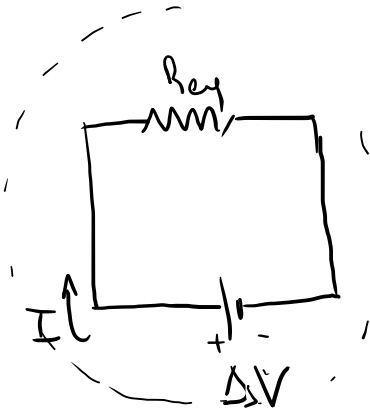

$$I = \frac{\Delta V}{R_{eq}}$$

$$\Delta V = \Delta V_1 = \Delta V_2$$

$$\frac{\Delta V}{R_{eq}} = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_m}$$

$$I = I_1 + I_2 \\ \downarrow \quad \downarrow \\ \frac{\Delta V}{R_{eq}} \quad \frac{\Delta V_1}{R_1} \quad \frac{\Delta V_2}{R_2}$$



leggi di Kirchhoff

$$\sum_{\text{nodo}} I = 0$$

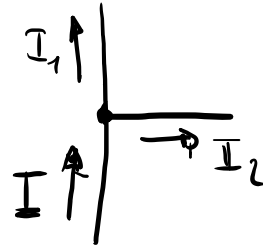

$$I + I_1 + I_2 = 0$$

$$\sum_{\text{maglie}} \Delta V = 0$$

